

Resistance

Resistance

- ▶ Resistance is opposition to the flow of current. A high resistance means it is harder for current to flow through. A low resistance means current will flow through more easily.
- ▶ Resistance is measured in **Ohms (Ω)**.

Ohm's Law

- ▶ Ohm's law states that current is directly proportional to potential difference at a constant temperature.

$$\text{Voltage} = \text{Current} \times \text{Resistance}$$

$$V = I \times R$$

- ▶ **Where:**

V = Voltage (Volts)

I = Current (Amps)

R = Resistance (Ω)

- ▶ Resistance of some resistor and component change like filament lamp or diode etc
- ▶ When electric charge flow through a lamp, it transfer energy to the thermal energy store of lamp. Due to this energy transfer the lamp get heat up.
- ▶ Resistance is directly proportional to Temperature and current. As temperatures increase, resistant and current also increases.
- ▶ For diodes: Resistant depend on the direction of the current, Current flow in one direction happily but if it is reversed, resistance gets high.

Types of Resistors

- ▶ Resistance in the circuit slows down the flow of charge (the current). For any given voltage, a higher resistance means a lower current. Resistance is measured in **ohms (Ω)**.

P2: Electricity. ASM Tuition Academy

- There are two different types of **resistors**, which are both able to slow down the current in a circuit:
 - **Fixed resistors** – fixed resistors have a constant value. Therefore, the resistance provided by a fixed resistor is constant.
 - **Variable resistors** – variable resistors do not have a fixed value – they can change their value as the current changes.
- **Components** in a circuit, such as lamps, will act as **variable** resistors. They are variable because their resistance will change depending on the current that flows through them.

Investigating the Resistance of Circuits

We can investigate the **factors** affecting resistance of circuits using the following method.

Method

1. **Construct a circuit** by Using an ammeter, voltmeter, switch and a variable resistor, set up the circuit shown below. Add a length of wire to the circuit, which should be movable as shown below.

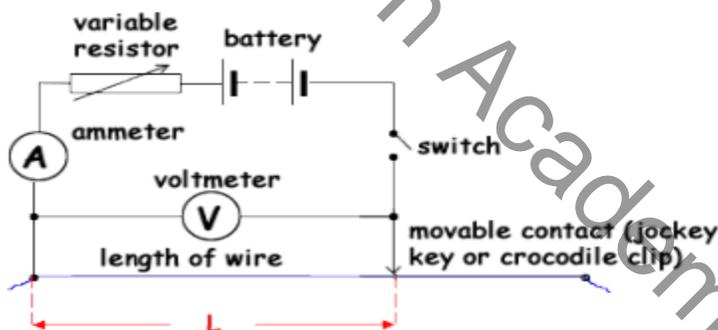


Fig 3. Example of a Constructed Circuit for This Experiment. There is a voltmeter, ammeter, resistor, switch and battery. The voltmeter is attached in parallel, whereas the other components are in series.

2. **Place the length of wire on a metre ruler.**The wire should stay at a constant temperature throughout the experiment.
3. **Measure 10cm of wire and** Attach crocodile clips on either end of the 10cm, so it is part of the circuit. .
4. **Record the current and pd (potential difference).** After closing the switch and completing the circuit, you can measure the current through the wire using the ammeter

P2: Electricity. ASM Tuition Academy

and the pd across the wire using the voltmeter. Record the current in amps and the potential difference in volts.

5. **Calculate the resistance.** Now that you have the current and potential difference, you can calculate the resistance. Do this by rearranging $V = IR$ into $R = V / I$. Record the resistance in ohms.

6. **Change the length of wire.** Once you have made the recordings for the 10cm length of wire, measure out a new section of wire. The new section should be 20cm. Repeat again step 4.

7. **Repeat the steps 3 to 6 of the experiment** with a slight alteration. Every time you repeat the experiment you should increase the length of wire by 10 cm. Record your results in a table like this

Length of wire (cm)	Current (Amps)	PD (Volts)	Resistance (Ohms)
10			
20			
30			

Table 2. Example Results Table for This Experiment.

8. **Repeat the experiment at least 6 times with different lengths**

9. **Plot a graph**, we can split a graph of wire length (x axis) against resistance (y axis). This graph should be a straight line through the origin. Here is an example graph:

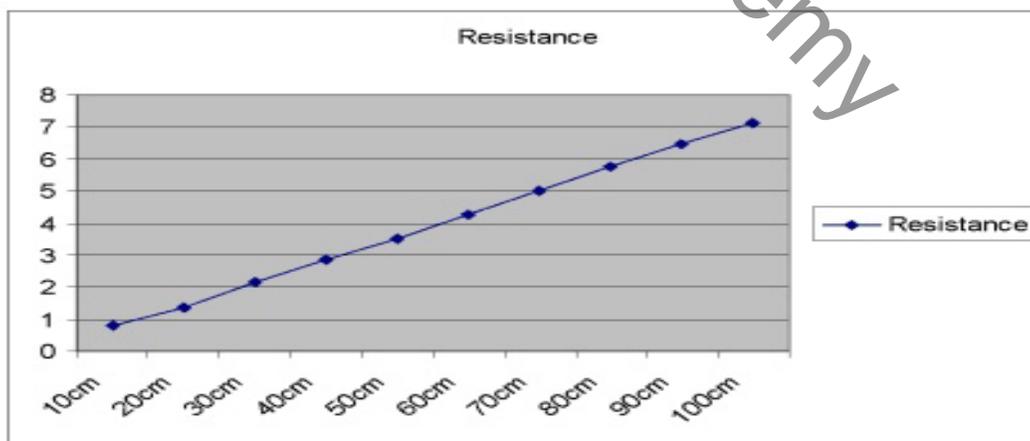


Table 3. Example Results Graph for This Experiment.

Current-Voltage Graphs—I-V characteristics

- ▶ **Ohm's Law** is a special relationship between current and potential difference of a component.
- ▶ The **term I-V graph refer** to graph which shows how current (I) flowing through component changes as the potential difference is increases.

Ohmic Conductor

- ▶ An **Ohmic conductor** is one that obeys Ohm's Law. As previously mentioned, Ohm's Law will give a straight line through origin, as shown in the **current-voltage graph** below.
- ▶ This graph would be produced by a **linear** circuit. A linear circuit is one which produces a straight line graph and obeys Ohm's Law.

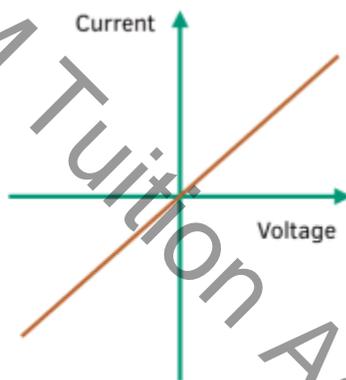


Fig 1. Current-Voltage Graph For an Ohmic Conductor. This is a straight line graph, through the origin. Therefore current is directly proportional to the voltage (assuming a constant temperature and resistance).

Filament Lamp

- ▶ Filament lamp has a filament inside it. As the **temperatures** of the filament increases, the **resistance** of the filament lamp will also increase.
- ▶ This graph would be produced by a **non-linear circuit**. A non linear circuit is one which does not produce a straight line current-voltage graph, but instead produces a curved line

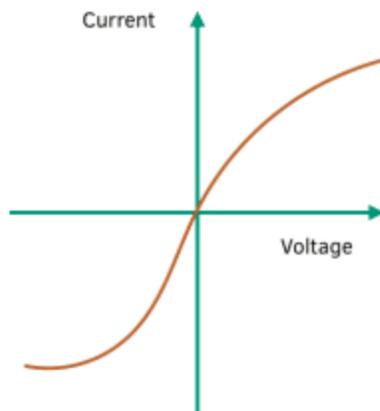


Fig 2. Current-Voltage Graph For a Filament Lamp.

Diodes

- ▶ **Diodes** are unique, since they only allow current to flow through them in one direction. The reason behind this is to do with resistance.
- ▶ Within a diode, there are 2 pathways of resistance. One has **very low resistance**, whilst the other has **very high resistance**. Current always flows through the path with the least resistance.
- ▶ This graph would be produced by a **non-linear circuit**. Remember, non linear circuit is one which produces a curved line.

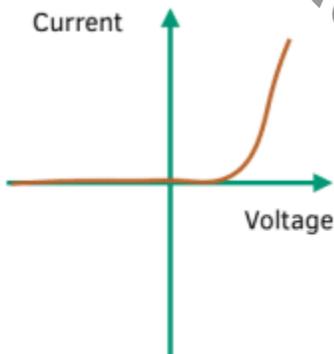


Fig 3. Current-Voltage Graph For a Diode. The graph shows that increasing the voltage one way will lead to a rise in current (after a certain voltage). However increasing the voltage the other way does not lead to a rise in current. The diode only works one way.

ASM Tuition Academy